

## Electrical and Electronics Engineering

### EEE2102

### Circuit Theory II


#### Experiment 1: AC Analysis Using PSPICE

**Objective:** To introduce PSPICE package program, view the magnitudes and phase relationships of sinusoidal voltage and current waveforms in an AC circuit.

#### Description

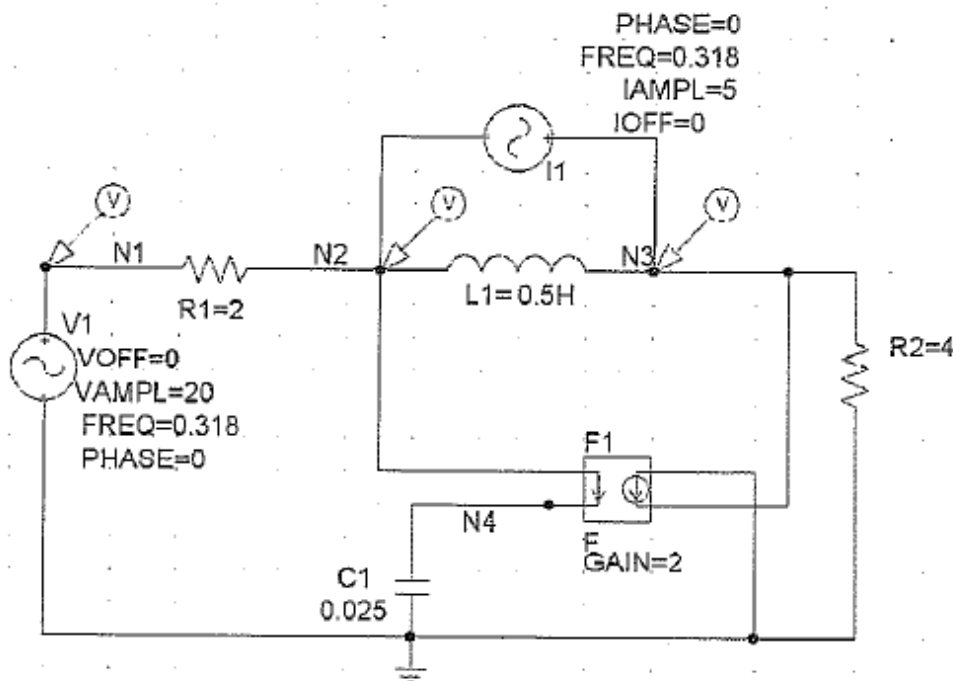**Phase relationships between the node voltages.**

- Construct the PSPICE schematics diagram given circuit below
- For the independent sources, use source type VSIN and ISIN
- Go to ANALYSIS and choose from the SETUP section the TRANSIENT analysis. Then set Print Step = 0.001 and Final Time = 16
- Insert the voltage probes to the three nodes
- Observe the voltage waveforms magnitudes of  $V_1$ ,  $V_2$  and  $V_3$  and phase difference
- Check to see whether  $V_2$  and  $V_3$  are leading or lagging  $V_1$



## Part II: Phase relationships between the branch currents

- Construct the PSPICE schematics diagram given circuit below
- For the independent sources, use source type VSIN and ISIN
- Insert the current probes to observe the circuit currents
- Find the period T and calculate the frequency
- Between I(I1) and I(L1) which is leading?

